
SECTION 22

POWER ELECTRONICS

Amit Kumar Jain

Engineering Technical Staff, Analog Power Design Inc.

Raja Ayyanar

Associate Professor, Department of Electrical Engineering, Arizona State University

CONTENTS

22.1	INTRODUCTION	22-2
22.1.1	Role of Power Electronic Converters	22-2
22.1.2	Application Examples	22-2
22.1.3	Scope and Organization	22-4
22.2	PRINCIPLES OF SWITCHED MODE POWER CONVERSION	22-4
22.2.1	Bipositional Switch	22-4
22.2.2	Pulse Width Modulation	22-5
22.2.3	Concept of Steady State	22-6
22.2.4	Power Loss in the Bipositional Switch	22-8
22.3	DC-DC CONVERTERS	22-9
22.3.1	Buck Converter	22-9
22.3.2	Boost Converter	22-12
22.3.3	Flyback Converter	22-13
22.3.4	Full-Bridge DC-DC Converter	22-14
22.3.5	Other Isolated DC-DC Converters	22-14
22.3.6	Recent Developments and Future Trends	22-16
22.4	FEEDBACK CONTROL OF POWER ELECTRONIC CONVERTERS	22-16
22.4.1	Dynamic Modeling	22-17
22.4.2	Control Design	22-19
22.4.3	Current Mode Control	22-21
22.4.4	Other Control Techniques	22-21
22.5	DC-AC CONVERSION: INVERSION	22-22
22.5.1	Single Phase AC Synthesis	22-22
22.5.2	Three-Phase AC Synthesis	22-25
22.5.3	Space Vector Modulation	22-26
22.5.4	Multilevel Converters	22-27
22.6	AC-DC CONVERSION: RECTIFICATION	22-30
22.6.1	Single-Phase Diode Bridge Rectifier	22-30
22.6.2	Three-Phase Diode Bridge Rectifier	22-32
22.6.3	Controlled Thyristor Rectifiers	22-34
22.7	AC TO AC CONVERSION	22-35
22.8	PROBLEMS CAUSED BY POWER ELECTRONIC CONVERTERS AND SOLUTIONS	22-37
22.8.1	Harmonics and Power Factor Correction	22-37
22.8.2	Electromagnetic Interference	22-40
22.9	APPLICATIONS OF POWER ELECTRONIC CONVERTERS	22-41
22.9.1	DC Power Supplies	22-41
22.9.2	Electric Drives	22-42
22.9.3	Battery Charging	22-45